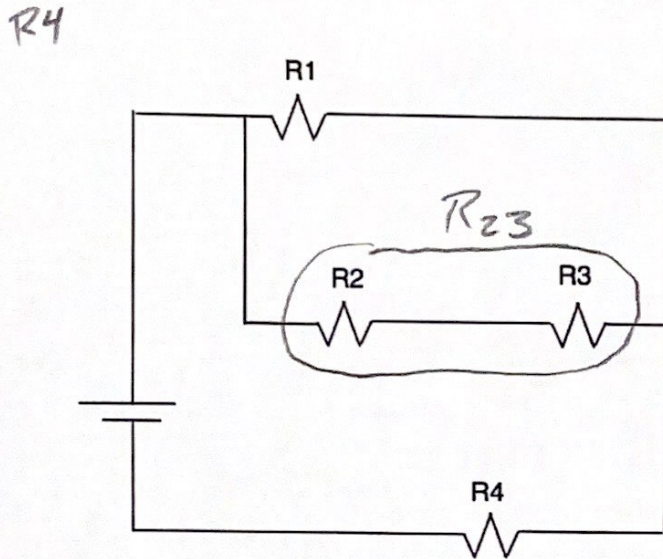


Quiz 20.1B

A 12.0-Volt battery is connected to a circuit as shown below. $R_1 = 1.52 \text{ Ohms}$, $R_2 = 2.35 \text{ Ohms}$, $R_3 = 3.41 \text{ Ohms}$, $R_4 = 4.45 \text{ Ohms}$.

- What is the equivalent resistance of the circuit?
- What is the current passing through resistor R_1 ?
- If R_2 is removed from the circuit, does your answer to (b) increase, decrease or remain the same? Justify your answer.




Series

$$R_{23} = R_2 + R_3 \\ = 5.76 \Omega$$

Parallel:
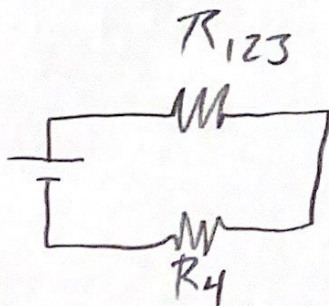
$$\frac{1}{R_1} + \frac{1}{R_{23}} = \frac{1}{R_{123}} \\ \Rightarrow R_{123} = 1.20 \Omega$$



Series

$$R_{TOT} = R_{123} + R_4 \\ = 5.65 \Omega$$

$$b) I_{TOT} = \frac{12}{R_{TOT}} = 2.12 \text{ A}$$

$$\Rightarrow I_{123} = 2.12 \text{ A}$$

$$\Rightarrow \Delta V_{123} = I_{123} R_{123} = 2.55 \text{ V}$$

$$\Rightarrow \Delta V_1 = 2.55 \text{ V}$$

$$I_1 = \frac{\Delta V_1}{R_1} = 1.68 \text{ A}$$

$$c) R_{TOT} \text{ now } 1.20 \Omega$$

so $I_{TOT} = \text{larger}$

still split same way,

so I_1 also larger