

Quiz 20.1C

A $125\ \mu\text{F}$ capacitor and an unknown resistor are connected in series with a $78.0\ \text{V}$ power source. At $t = 0.00\ \text{s}$, a switch is closed to complete the circuit, and the capacitor begins to charge. A student determines that the voltage drop across the capacitor after $1.33\ \text{s}$ is $38.0\ \text{V}$.

- a) What is the charge on the capacitor at this time?
- b) What is the time constant of this circuit?
- c) What is the resistance of the resistor in this circuit?
- d) At $t = 1.33\ \text{s}$, what is the current in the circuit?