
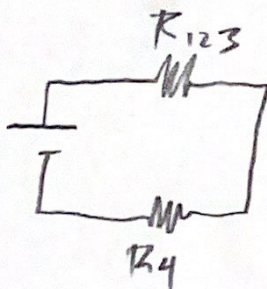


Quiz 20.1D

A 12.0-Volt battery is connected to a circuit as shown below. $R_1 = 1.22 \text{ Ohms}$, $R_2 = 2.55 \text{ Ohms}$, $R_3 = 3.21 \text{ Ohms}$, $R_4 = 4.75 \text{ Ohms}$.

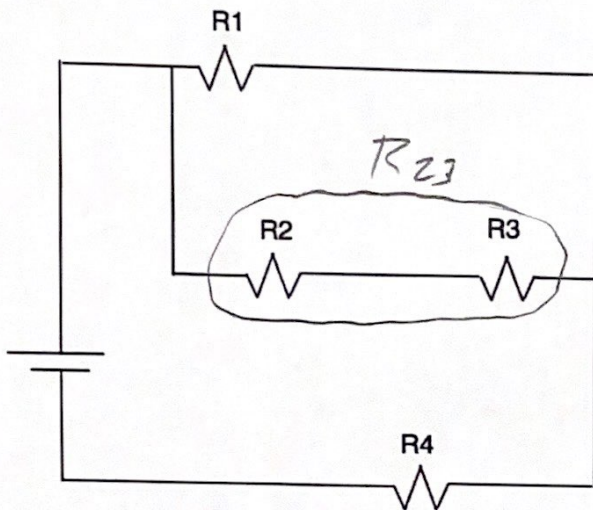- What is the equivalent resistance of the circuit?
- What is the current passing through resistor R_3 ?
- If R_1 is removed from the circuit, does your answer to (b) increase, decrease or remain the same? Justify your answer.



- c) If no R_1 , $R_{TOT} = R_2 + R_3 + R_4$
 $= 10.51 \Omega$

$$I_{TOT} = 1.14 \text{ A}$$

$$\Rightarrow I_3 = 1.14 \text{ A} \text{ / increase}$$

Series

$$R_{23} = R_2 + R_3 = 5.76 \Omega$$

Parallel

$$\frac{1}{R_{123}} = \frac{1}{R_1} + \frac{1}{R_{23}}$$

$$\Rightarrow R_{123} = 1.01 \Omega$$

Series

$$R_{TOT} = R_{123} + R_4 = \boxed{5.76 \Omega}$$

$$I_{TOT} = \frac{E}{R_{TOT}} = 2.08 \text{ A}$$

$$\Rightarrow I_{123} = 2.08 \text{ A}$$

$$\Rightarrow \Delta V_{123} = IR = 2.11 \text{ V}$$

$$\Rightarrow \Delta V_{23} = 2.11 \text{ Volts}$$

$$\Rightarrow I_{23} = \frac{\Delta V}{R} = 0.366 \text{ A}$$

$$\Rightarrow \boxed{I_3 = 0.366 \text{ A}}$$