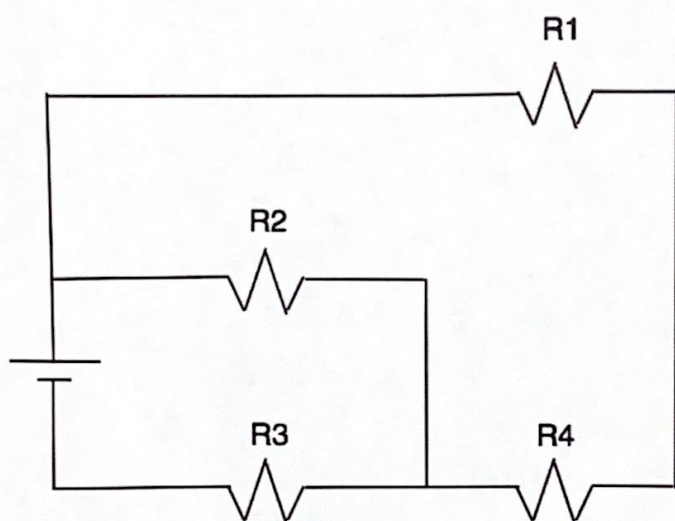


### Quiz 20.1E


A 12-Volt battery is connected to a circuit as shown below.  $R_1 = 1.3 \text{ Ohms}$ ,  $R_2 = 2.2 \text{ Ohms}$ ,  $R_3 = 3.6 \text{ Ohms}$ ,  $R_4 = 4.1 \text{ Ohms}$ .

- What is the equivalent resistance of the circuit?
- What is the current passing through resistor  $R_4$ ?
- If  $R_2$  is removed from the circuit, does your answer to (b) increase, decrease or remain the same? Justify your answer.



Series

$$R_{14} = R_1 + R_4 = 5.4 \Omega$$

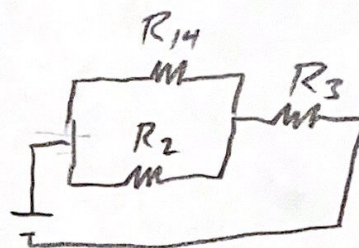

Parallel

$$\frac{1}{R_{142}} = \frac{1}{5.4} + \frac{1}{2.2}$$

$$\Rightarrow R_{142} = 1.56 \Omega$$

Series:  $R_{142} + R_3 = R_{TOT} = 5.2 \Omega$

b)  $I_{TOT} = \frac{\mathcal{E}}{R_{TOT}} = 2.32 \text{ A} \Rightarrow \Delta V_{142} = I_{142} R_{142} = 3.63 \text{ V}$   
 $= I_{142} = I_3 \Rightarrow \Delta V_{14} = 3.63 \text{ V}$

$$\Rightarrow I_{14} = \frac{\Delta V_{14}}{R_{14}} = \frac{3.63}{5.4} = 0.67 \text{ A}$$

c) If no  $R_2$ ,  $R_{TOT} = R_1 + R_4 + R_3$   
 $= 9.0 \Omega$

$$\Rightarrow I_4 = 0.67 \text{ A}$$

$$\Rightarrow I_{TOT} = \frac{\mathcal{E}}{9} = 1.33 \text{ A} \Rightarrow I_4 = 1.33 \text{ A, increases}$$