

Ch 20 HW Quiz #2A

For the circuit below,

- Determine the power dissipated by the resistor R_2 when the switch S is closed.
- If the switch is opened, does your answer to (a) increase, decrease or remain the same? Justify your answer.

